Obstacle Avoidance Robot

Components Used:

- 1. **Arduino** (1 unit)
- 2. H-bridge (1 unit)
- 3. HC-SR04 Ultrasonic Sensor (1 unit)
- 4. **DC Motors** (4 units)
- 5. Batteries (3 units)
- 6. Wires and connectors
- 7. Chassis
- 8. Breadboard

Hardware Connections:

Pin Assignments:

Component	Pin Description	Arduino Pin
Left Motor	Direction Control	Pin 4 (rev) & Pin 5 (fwd)
Right Motor	Direction Control	Pin 7 (rev) & Pin 6 (fwd)
Ultrasonic Sensor	Trig Pin	Pin 10
	Echo Pin	Pin 9

Step-by-Step Hardware Connections:

- 1. Connecting the Motors:
 - Connect the left motor's positive terminal to OUT1 on the H-bridge
 - Connect the left motor's negative terminal to OUT2 on the H-bridge
 - Connect the right motor's positive terminal to OUT3 on the H-bridge
 - o Connect the right motor's negative terminal to OUT4 on the H-bridge
- 2. Connecting Motor Driver to Arduino:
 - o Connect **IN1** (**H-bridge**) to **pin 4** on the Arduino (Reverse left motor).
 - Connect IN2 (H-bridge) to pin 5 on the Arduino (Forward left motor).
 - Connect **IN3** (**H-bridge**) to **pin 7** on the Arduino (Reverse right motor).
 - Connect IN4 (H-bridge) to pin 6 on the Arduino (Forward right motor).
- 3. Powering the Motor Driver:
 - Connect the +12V pin of the H-bridge to the positive terminal of the battery pack.
 - Connect the GND pin of the H-bridge to the GND of the battery pack (common ground).
 - Connect the 5V pin from the H-bridge to the 5V pin on the Arduino for powering the Arduino.
- 4. Connecting Ultrasonic Sensor (HC-SR04) to Arduino:

- o **Trig Pin** (HC-SR04) is connected to **pin 10** on the Arduino Mega.
- o **Echo Pin** (HC-SR04) is connected to **pin 9** on the Arduino Mega.
- o **VCC** is connected to **5V** on the Arduino Mega.
- $\circ\quad$ GND is connected to GND on the Arduino Mega.