

# Obstacle Avoidance Robot

## Components Used:

1. **Arduino Uno** (1 unit)
  2. **H-bridge** (1 unit)
  3. **Ultrasonic Sensors (HC-SR04)** (3 units - Left, Front, and Right)
  4. **Motors** (4 units)
  5. **Batteries** (3 units)
  6. **Wires and connectors**
  7. **Chassis**
  8. **Breadboard**
- 

## Pin Assignments:

Component	Pin Description	Arduino Pin
<b>Left Motor</b>	Direction Control 1	Pin 3
	Direction Control 2	Pin 5
<b>Right Motor</b>	Direction Control 1	Pin 6
	Direction Control 2	Pin 9
<b>Left Ultrasonic Sensor</b>	Trig Pin	Pin 2
	Echo Pin	Pin 4
<b>Front Ultrasonic Sensor</b>	Trig Pin	Pin 7
	Echo Pin	Pin 8
<b>Right Ultrasonic Sensor</b>	Trig Pin	Pin 10
	Echo Pin	Pin 11

---

## Hardware Connections:

### 1. Connecting the Motors:

The two **DC motors** will be connected to the **L298N Motor Driver** for speed and direction control.

- Connect the **left motor's positive terminal** to **OUT1** on the H-bridge.
- Connect the **left motor's negative terminal** to **OUT2** on the H-bridge.
- Connect the **right motor's positive terminal** to **OUT3** on the H-bridge.
- Connect the **right motor's negative terminal** to **OUT4** on the H-bridge.

## 2. Connecting Motor Driver to Arduino:

The H-bridge **motor driver** receives control signals from the **Arduino** for the direction and speed of the motors:

- Connect **IN1** (L298N) to **pin 3** on the Arduino.
- Connect **IN2** (L298N) to **pin 5** on the Arduino.
- Connect **IN3** (L298N) to **pin 6** on the Arduino.
- Connect **IN4** (L298N) to **pin 9** on the Arduino.

These pins control the direction and speed of the left and right motors.

## 3. Powering the Motor Driver:

- Connect the **+12V pin** of the **L298N motor driver** to the **positive terminal of the battery pack**.
- Connect the **GND pin** of the L298N motor driver to the **GND of the battery pack** (common ground).
- Connect the **5V pin** from the L298N motor driver to the **5V pin** on the **Arduino** for powering the Arduino.

## 4. Connecting Ultrasonic Sensors to Arduino:

Use three **HC-SR04 ultrasonic sensors** to detect obstacles from the left, front, and right.

- **Left Ultrasonic Sensor:**
  - Connect the **Trig** pin to **pin 2** on the Arduino.
  - Connect the **Echo** pin to **pin 4** on the Arduino.
- **Front Ultrasonic Sensor:**
  - Connect the **Trig** pin to **pin 7** on the Arduino.
  - Connect the **Echo** pin to **pin 8** on the Arduino.
- **Right Ultrasonic Sensor:**
  - Connect the **Trig** pin to **pin 10** on the Arduino.
  - Connect the **Echo** pin to **pin 11** on the Arduino.

## 5. Powering the Ultrasonic Sensors:

- Connect the **VCC pin** of each ultrasonic sensor to the **5V pin** on the Arduino.
- Connect the **GND pin** of each ultrasonic sensor to the **GND pin** on the Arduino.

## 6. Power Supply for Arduino:

- The Arduino is powered through the **5V pin** from the L298N motor driver.
  - Ensure that the **GND pin** of the Arduino is connected to the **common ground** shared by the L298N motor driver and the ultrasonic sensors.
-